

---

# Lecture 7 FSM Design

7.1 Modeling Finite State Machine

7.2 Mealy and Moore FSMs with Verilog Design

7.3 Design Example: Sequence Detector

7.4 Design Example: Odd/Even Number of 1's Checker

7.5 Design Example: Data Package Receiver

## 7.1 Modeling Finite State Machine

## 7.2 Mealy and Moore FSMs with Verilog Design


## 7.3 Design Example: Sequence Detector

## 7.4 Design Example: Odd/Even Number of 1's Checker

## 7.5 Design Example: Data Package Receiver

## 7.1.1 Introduction to FSM

- Finite State Machine (FSM)
  - A design component that demonstrates behavior characterized by a finite set of states
    - Combinational circuits: next state and the output
    - Sequential circuit: registers to 1) memorize the status/states; 2) isolate `cur_state` from the `nxt_state` for timing control
- Template for coding a Finite State Machine (FSM)
  - Sequential circuit: register
  - Combinational circuit of the `nxt_state`: *always* block
  - Combinational circuit of the output: *assign/always* blocks

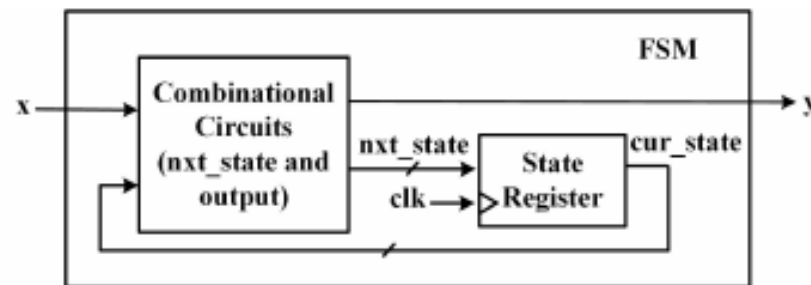

**FIGURE 7.1**  
Finite State Machine Model

## 7.1.2 FSM Template with Verilog HDL

- State register
  - Encoding: 4 states so 2-bit width of the *parameter* SIZE
  - One-hot encoding: S0=4'b0001, S1=4'b0010, S2=4'b0100, and S3=4'b1000.
    - Advantage: Only one state bit ON at a time.
    - Downside: Takes more flip flops.

```
1  module FSM_template (input      rst      ,
2                        input      clk      ,
3                        input      x        ,
4                        output reg y       );
5  parameter SIZE = 2;
6  parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3=2'b11;
7
8  reg [SIZE-1:0] cur_state; // Sequential part of the FSM
9  reg [SIZE-1:0] nxt_state; // Combinational part of the FSM
10
11 //-----State Register -----
12 always @ (posedge clk, negedge rst) begin
13     if (~rst) begin
14         cur_state <= S0;
15     end else begin
16         cur_state <= nxt_state;
17     end
18 end
```

## 7.1.2 FSM Template with Verilog HDL

- Combinational circuit of the next state
- Combinational circuit of the output y
  - The output design could be simplified using *assign* blocks. In such a case, the output signal ``y" must be declared as a *wire* data type.

```
20 //---- Combinational Circuit for the Next State ---
21 always @ (cur_state, x, rst) begin
22     if (~rst) begin
23         nxt_state <= S0;
24     end else begin
25         case(cur_state)
26             S0      :
27             S1      :
28             S2      :
29             S3      :
30             default: nxt_state <= S0;
31         endcase
32     end
33 end
34
```

```
35 //-----Output Combinational Circuit-----
36 always @ (cur_state, x, rst) begin
37     if (~rst) begin
38         y <= 1'b0;
39     end else begin
40         case(cur_state)
41             S0      :
42             S1      :
43             S2      :
44             S3      :
45             default: y <= 1'b0;
46         endcase
47     end
48 end
49 endmodule
```

7.1 Modeling Finite State Machine

7.2 Mealy and Moore FSMs with Verilog Design


7.3 Design Example: Sequence Detector

7.4 Design Example: Odd/Even Number of 1's Checker

7.5 Design Example: Data Package Receiver

## 7.2.1 Introduction to Mealy and Moore Machine

- Mealy machine:
  - The outputs are associated with both the current state and the inputs during the transition.
- Moore machine:
  - The outputs are solely dependent on the current state and are not influenced by the inputs.

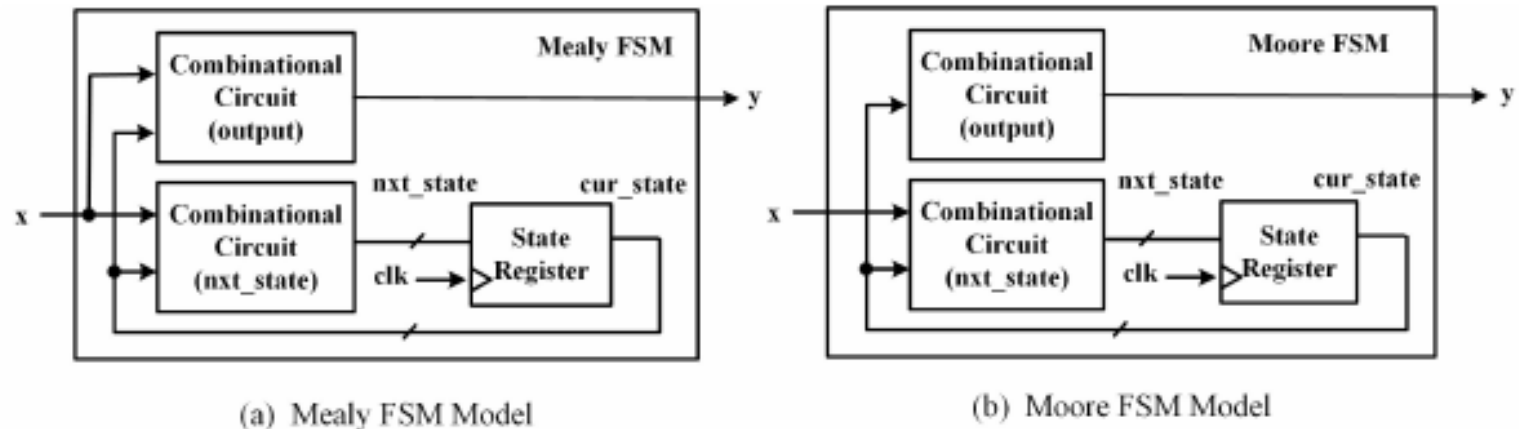


**FIGURE 7.2**  
Mealy and Moore FSM Models



## 7.2.1 Introduction to Mealy and Moore Machine


- Designing and evaluating an FSM
  - 1) Constructing a state graph
  - 2) Creating the state table and encoding it into a transition table
    - Synthesis tools in the IC design process can automate the K-map optimization, thus removing the necessity for manual K-map optimization by RTL designers)
  - 3) Designing the FSM using Verilog HDL
  - 4) Analyzing the simulation and synthesis results using Karnaugh maps (commonly known as K-maps).

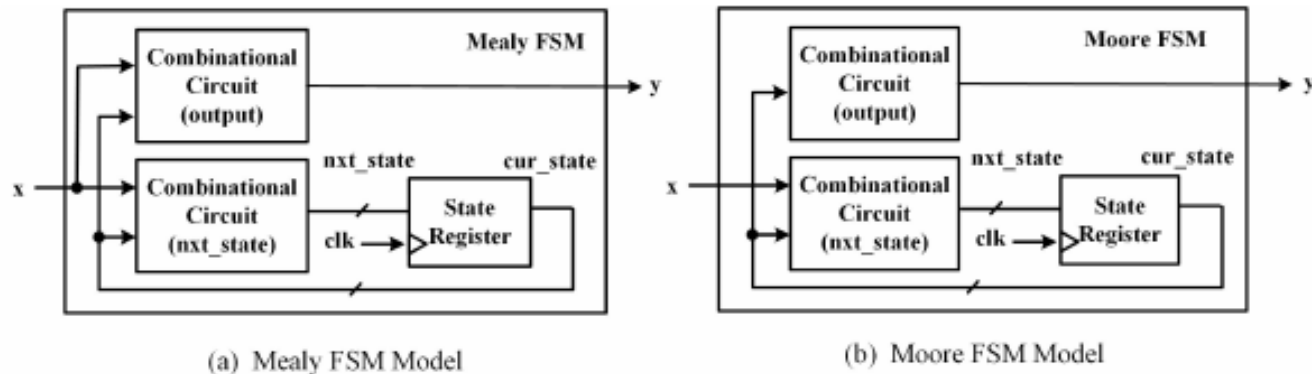

**FIGURE 7.2**  
Mealy and Moore FSM Models

## 7.2.2.1 State Graph of Mealy Machine

- State graph
  - Three current states, represented by circles labeled as ``S0'', ``S1'', and ``S2''.
    - When the circuit is reset, the state machine initializes to the initial state, ``S0''.
  - The arcs connecting the current states to the next states represent the state transitions that occur over clock cycles.
    - In every clock cycle, one of the arcs will be executed to transition the machine state into the next state.
  - Each arc also includes the input ``x'' and its corresponding output ``y''.
    - The output ``y'' is determined based on the current states (in the circle) and the input ``x'' (on the arc).

 


**FIGURE 7.3**

 State Graph of Mealy FSM

## 7.2.2.2 State and Transition Tables of Mealy Machine

- State table and Transition table
  - The transition table is presented by encoding the state table.
  - As there are three states being represented, a 2-bit register is required.
    - The `q1` and `q0` bits refer to the Most Significant Bit (MSB) and Least Significant Bit (LSB) of the current state, respectively. On the other hand, `q1+` and `q0+` represent the MSB and LSB of the next state.
    - The next state (`q1+q0+`) serves as the input to the state register, while the current state (`q1q0`) serves as the output of the state register.



cur_state	nxt_state		y	
	x=0	x=1	x=0	x=1
S0	S0	S1	0	0
S1	S2	S1	0	0
S2	S0	S1	0	1

(a) State Table of the Mealy FSM

q1q0	q1+q0+		y	
	x=0	x=1	x=0	x=1
00	00	01	0	0
01	10	01	0	0
10	00	01	0	1

S0=2'b00, S1=2'b01, S2=2'b10


(b) Transition Table of the Mealy FSM

**FIGURE 7.4**

State and Transition Tables of Mealy FSM
 
## 7.2.2.3 Verilog HDL Design of Mealy Machine



```
1 module mealy_fsm(input    rst      ,
2                  input    clk      ,
3                  input    x        ,
4                  output   y        );
5
6 parameter SIZE = 2;
7 parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10;
8
9 reg [SIZE-1:0] cur_state; // Sequential part of the FSM
10 reg [SIZE-1:0] nxt_state; // Combinational part of the FSM
11
12 //-----State Register -----
13 always @ (posedge clk, negedge rst) begin
14     if (~rst) begin
15         cur_state <= S0;
16     end else begin
17         cur_state <= nxt_state;
18     end
19 end
20
21 //-----Next State Combinational Circuit--
22 always @ (cur_state, x, rst) begin
23     if (~rst) begin
24         nxt_state = S0;
25     end else begin
26         case(cur_state)
27             S0    : if(x)  nxt_state=S1;
28             S1    : if(~x)  nxt_state=S2;
29             S2    : if(x)  nxt_state=S1; else nxt_state=S0;
30             default: nxt_state = S0;
31         endcase
32     end
33 end
34
35 //-----Output Combinational Circuit-----
36 assign y = (cur_state==S2) & x;
37 endmodule
```



- Verilog code to describe the mealy machine
  - The missing *else* in each case statement represents the scenario where the next state stays the same as the current state.
  - The computation of the output ``y" is described using a concurrent *assign* block in lines 35-36. Therefore, the output ``y" is declared in line 4 in a default *wire* data type.

## 7.2.2.4 Simulation and Synthesis Analysis of Mealy Machine

- A. Synthesized Circuit
- B. Timing Diagram

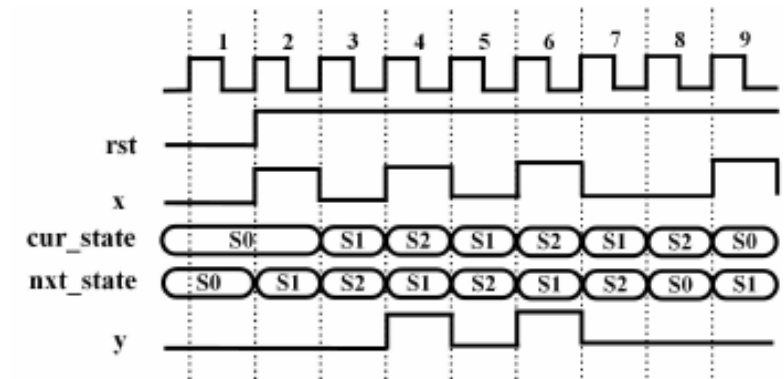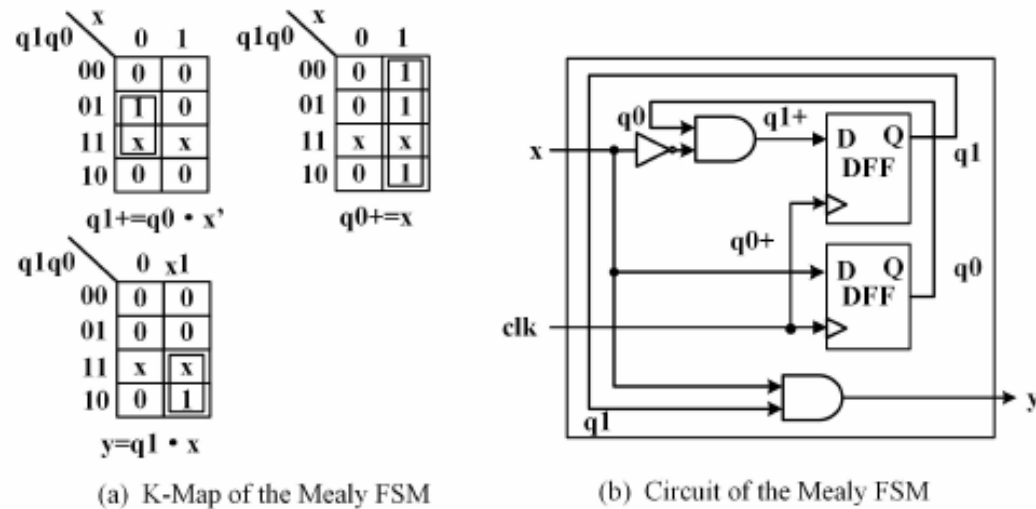

**FIGURE 7.6**  
Timing Diagram of Mealy FSM

**FIGURE 7.5**  
K-Map Optimization and Circuit of Mealy FSM

cur_state	nxt_state		y	
	x=0	x=1	x=0	x=1
S0	S0	S1	0	0
S1	S2	S1	0	0
S2	S0	S1	0	1



(a) State Table of the Mealy FSM

q1q0	q1+q0+		y	
	x=0	x=1	x=0	x=1
00	00	01	0	0
01	10	01	0	0
10	00	01	0	1

S0=2'b00, S1=2'b01, S2=2'b10

(b) Transition Table of the Mealy FSM

# Timing Diagram Analysis

 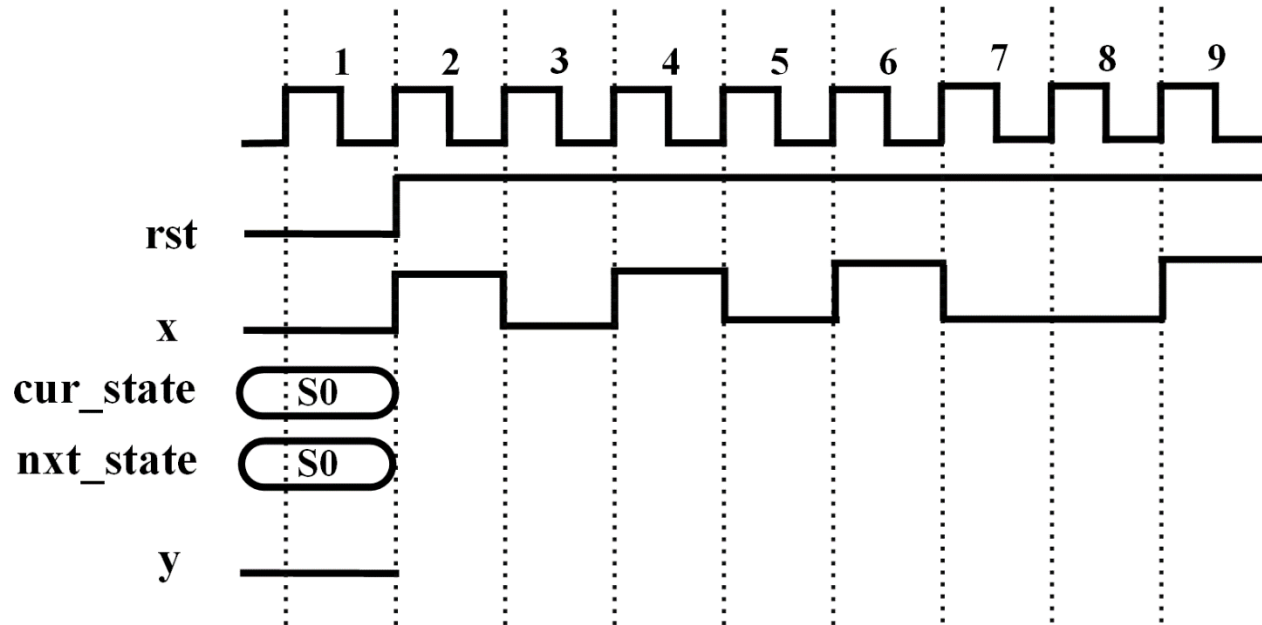

cur_state	nxt_state		y	
	x=0	x=1	x=0	x=1
S0	S0	S1	0	0
S1	S2	S1	0	0
S2	S0	S1	0	1

q1q0	q1+q0+		y	
	x=0	x=1	x=0	x=1
00	00	01	0	0
01	10	01	0	0
10	00	01	0	1


S0=2'b00, S1=2'b01, S2=2'b10

(a) State Table of the Mealy FSM

(b) Transition Table of the Mealy FSM

## 7.2.3.1 State Graph of Moore Machine


- State graph
  - The current states ("S0", "S1", "S2", and "S3") and the output "y" are all represented within the four circles.
    - Because in a Moore machine the output "y" depends solely on the current state and remains constant within each state.
    - Consequently, it takes an additional state, "S3", to represent the output "y=1" compared to a Mealy machine.
  - The arcs connecting the current states to the next states represent the transitions that happen over clock cycles.

 

**FIGURE 7.7**  
State Graph of Moore FSM
 
## 7.2.3.2 State and Transition Tables of Moore Machine

- State table
  - The output ``y" is solely determined by the current state. Therefore, the last column displays the output ``y" without considering the input ``x".
- Transition table
  - The transition of the next state (``q1+q0+") is determined by the combination of the current state (``q1q0") and the input ``x".



cur_state	nxt_state		y
	x=0	x=1	
S0	S0	S1	0
S1	S2	S1	0
S2	S0	S3	0
S3	S2	S1	1

q1q0	q1+q0+		y
	x=0	x=1	
00	00	01	0
01	10	01	0
10	00	11	0
11	10	01	1

S0=2'b00, S1=2'b01,  
S2=2'b10, S3=2'b11

(a) State Table of the Moore FSM      (b) Transition Table of the Moore FSM

**FIGURE 7.8**


State and Transition Tables of Moore FSM


 
## 7.2.3.3 Verilog HDL Design of Moore Machine


```
1 module moore_fsm(input      rst      ,
2                  input      clk      ,
3                  input      x        ,
4                  output     y        );
5
6 parameter SIZE = 2;
7 parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
8
9 reg [SIZE-1:0] cur_state; // Sequential part of the FSM
10 reg [SIZE-1:0] nxt_state; // Combinational part of the FSM
11
12 //-----State Register -----
13 always @ (posedge clk, negedge rst) begin
14     if (~rst) begin
15         cur_state <= S0;
16     end else begin
17         cur_state <= nxt_state;
18     end
19 end
20
21 //-----Next State Combinational Circuit-----
22 always @ (cur_state, x, rst) begin
23     if (~rst) begin
24         nxt_state = S0;
25     end else begin
26         case(cur_state)
27             S0 : if(x)  nxt_state=S1;
28             S1 : if(~x)  nxt_state=S2;
29             S2 : if(x)  nxt_state=S3; else nxt_state=S0;
30             S3 : if(x)  nxt_state=S1; else nxt_state=S2;
31             default: nxt_state = S0;
32         endcase
33     end
34 end
35
36 //-----Output Combinational Circuit-----
37 assign y = (cur_state==S3);
38 endmodule
```

- Verilog code to describe the mealy machine
  - The output ``y" is set to binary one only when the current state is ``S3". The output computation does not depend on the input ``x".




## 7.2.2 Simulation and Synthesis Analysis of Moore Machine

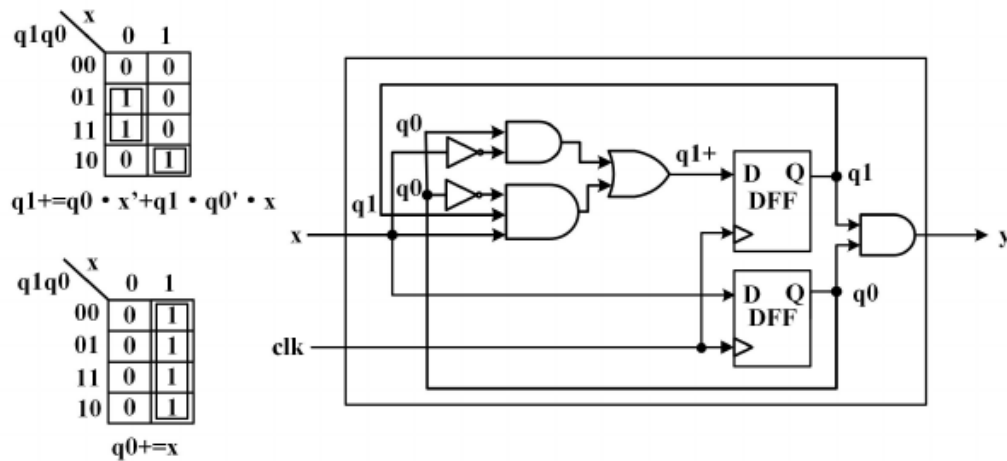- A. Synthesized Circuit
- B. Timing Diagram



(a) K-Map of the Moore FSM

(b) Circuit of the Moore FSM

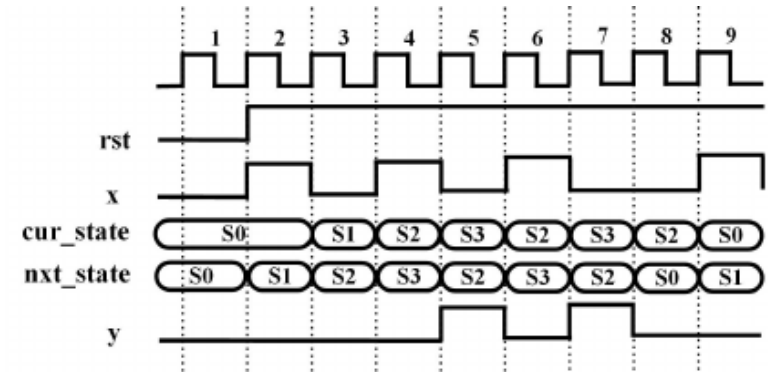

**FIGURE 7.10**  
Timing Diagram of Moore FSM

**FIGURE 7.9**  
K-Map Optimization and Circuit of Moore FSM

cur_state	nxt_state		y
	x=0	x=1	
S0	S0	S1	0
S1	S2	S1	0
S2	S0	S3	0
S3	S2	S1	1



(a) State Table of the Moore FSM

q1q0	q1+q0+		y
	x=0	x=1	
00	00	01	0
01	10	01	0
10	00	11	0
11	10	01	1

$S0=2'b00$ ,  $S1=2'b01$ ,  
 $S2=2'b10$ ,  $S3=2'b11$

(b) Transition Table of the Moore FSM

# Timing Diagram Analysis

  

cur_state	nxt_state		y	
	x=0	x=1	x=0	x=1
S0	S0	S1	0	0
S1	S2	S1	0	0
S2	S0	S1	0	1

(a) State Table of the Mealy FSM

q1q0	q1+q0+		y	
	x=0	x=1	x=0	x=1
00	00	01	0	0
01	10	01	0	0
10	00	01	0	1

S0=2'b00, S1=2'b01, S2=2'b10

(b) Transition Table of the Mealy FSM

7.1 Modeling Finite State Machine

7.2 Mealy and Moore FSMs with Verilog Design


**7.3 Design Example: Sequence Detector**

7.4 Design Example: Odd/Even Number of 1's Checker


7.5 Design Example: Data Package Receiver

## 7.3.1 Introduction to Sequence Detector

- Introduction to Sequence Detector
  - Asserts an output signal `y=1` when a specified pattern of consecutive bits is received in the serial input stream `x`.
  - The input stream is fed into the detector from left to right, with only one bit digit per clock cycle.

 

**FIGURE 7.11**  
A Sequence Detector

 

**FIGURE 7.12**  
Digit String of 0101 Sequence Detector with Mealy and Moore FSM

- The digits in the input can be overlapping between two consecutive occurrences of the desired 0101 string.

## 7.3.1 Introduction to Sequence Detector

---

- Introduction to Sequence Detector
  - The asynchronous reset is utilized for initializing the register,
  - The clock is employed to sample each digit input.
  - A state register is a crucial component in this design, responsible for storing and updating the status of the digit string input.
    - It ensures that the state can be updated on every active clock cycle, enabling the sequence detector to effectively track and detect the desired digit pattern.


**TABLE 7.1**

Sequence Detector IOs Description

Name	Direction	Bit Width	Description
clk	Input	1	Clock, rising edge trigger
rst	Input	1	Asynchronous reset, 0 valid
x	Input	1	Digit string input
y	Output	1	Output 1 when 0101 string detected

## 7.3.2.1 Mealy State Graph of 0101 Sequence Detector

- State graph
  - S0: initial state
    - From initial state, if 0 input remains to S0; if 1 input goes to S1
  - S1: the first desired 0 is received
    - From S1, if 0 input remains in S1; if 1 input goes to S2
  - S2: the two desired sequence 01 is received
    - From S2, if 0 input goes to S3; if 1 input goes to S0
  - S3: the three desired sequence 010 is received
    - From S3, if 0 input goes to S1; if 1 input goes to S2

 


**FIGURE 7.13**

 State Graph of 0101 Sequence Detector Design with Mealy FSM

## 7.3.2.2 Mealy State and Transition Tables of 0101 Sequence Detector

- State table
- Transition table
  - $q1+q0+$ : next state
  - $q1q0$ : current state
  - $y$ : output dependent on the input  $x$  and the current state  $q1q0$



cur_state	nxt_state		y	
	x=0	x=1	x=0	x=1
S0	S1	S0	0	0
S1	S1	S2	0	0
S2	S3	S0	0	0
S3	S1	S2	0	1

(a) State Table of the 0101 Sequence Detector Design with Mealy FSM

q1q0	q1+q0+		y	
	x=0	x=1	x=0	x=1
00	01	00	0	0
01	01	10	0	0
10	11	00	0	0
11	01	10	0	1

$S0=2'b00, S1=2'b01, S2=2'b10, S3=2'b11$

(b) Transition Table of the 0101 Sequence Detector Design with Mealy FSM

**FIGURE 7.14**

State and Transition Tables of 0101 Sequence Detector Design with Mealy FSM




## 7.3.2.3 Verilog HDL Design of 0101 Mealy Sequence Detector

```

1  module seq_det_0101_mealy (input  rst,
2                             input  clk,
3                             input  x ,
4                             output y );
5
6  parameter SIZE = 2;
7  parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
8
9  reg [SIZE-1:0] cur_state; // Sequential part of the FSM
10 reg [SIZE-1:0] nxt_state; // Combinational part of the FSM
11
12 //-----State Register -----
13 always @ (posedge clk, negedge rst) begin
14     if (~rst) begin
15         cur_state <= S0;
16     end else begin
17         cur_state <= nxt_state;
18     end
19 end
20
21 //-----Next state combinational circuit-----
22 always @ (cur_state, x, rst) begin
23     if (~rst) begin
24         nxt_state = 2'b00;
25     end else begin
26         case(cur_state)
27             S0:    if(~x) nxt_state = S1;
28             S1:    if(x)  nxt_state = S2;
29             S2:    if(~x) nxt_state = S3; else nxt_state = S0;
30             S3:    if(~x) nxt_state = S1; else nxt_state = S2;
31             default: nxt_state = S0;
32         endcase
33     end
34 end
35
36 //-----Output combinational circuit-----
37 assign y = (cur_state==S3) & x;
38 endmodule

```

 

- Verilog code to describe the mealy machine
  - The state register is described in lines 12-19, and the next state transitions is designed in lines 21-34.
  - In line 37, the output signal ``y" is asserted when the current state is ``S3" and the subsequent input ``x" is one, completing the desired digit string 0101.

## 7.3.2.4 Simulation and Synthesis Analysis of 0101 Mealy Sequence Detector


- A. Synthesized Circuit

q1q0 \ x	0	1
	00	01
00	0	0
01	0	1
11	0	1
10	1	0

$q1+ = q0 \cdot x + q1 \cdot q0' \cdot x'$

q1q0 \ x	0	1
	00	01
00	1	0
01	1	0
11	1	0
10	1	0

$q0+ = x'$

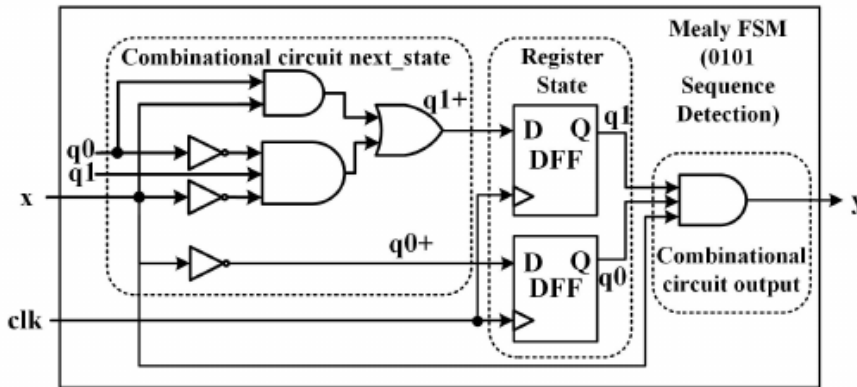

(a) K-Map of the 0101 Sequence Detector Design with Mealy FSM

(b) Circuit of the 0101 Sequence Detector Design with Mealy FSM

FIGURE 7.15

K-Map Optimization and Circuit of 0101 Sequence Detector Design with Mealy FSM

cur_state	nxt_state		y	
	x=0	x=1	x=0	x=1
S0	S1	S0	0	0
S1	S1	S2	0	0
S2	S3	S0	0	0
S3	S1	S2	0	1

(a) State Table of the 0101 Sequence Detector Design with Mealy FSM

q1q0	q1+q0+		y	
	x=0	x=1	x=0	x=1
00	01	00	0	0
01	01	10	0	0
10	11	00	0	0
11	01	10	0	1

S0=2'b00, S1=2'b01, S2=2'b10, S3=2'b11

(b) Transition Table of the 0101 Sequence Detector Design with Mealy FSM

## 7.3.2.4 Simulation and Synthesis Analysis of 0101 Mealy Sequence Detector

### • B. Timing Diagram

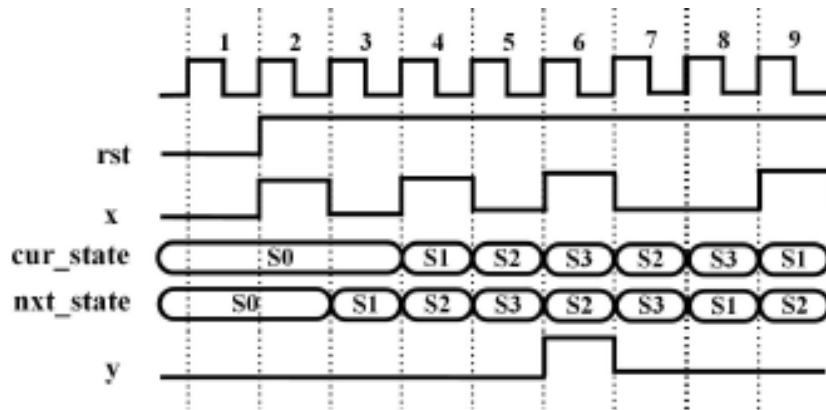


FIGURE 7.16

Timing Diagram of the 0101 Sequence Detector Design with Mealy FSM

cur_state	nxt_state		y	
	x=0	x=1	x=0	x=1
S0	S1	S0	0	0
S1	S1	S2	0	0
S2	S3	S0	0	0
S3	S1	S2	0	1

q1q0	q1+q0+		y	
	x=0	x=1	x=0	x=1
00	01	00	0	0
01	01	10	0	0
10	11	00	0	0
11	01	10	0	1

S0=2'b00, S1=2'b01, S2=2'b10, S3=2'b11

(a) State Table of the 0101 Sequence Detector Design with Mealy FSM

(b) Transition Table of the 0101 Sequence Detector Design with Mealy FSM

## 7.3.3.1 Moore State Graph of 0101 Sequence Detector

- State graph

- S0: initial state,  $y=0$

- From initial state, if 0 input goes to S1; if 1 input remains to S0

- S1: the 1st desired 0 is received,  $y=0$

- From S1, if 0 input remains in S1; if 1 input goes to S2

- S2: the 2 desired sequence 01 is received,  $y=0$

- From S2, if 0 input goes to S3; if 1 input goes to S0

- S3: the 3 desired sequence 010 is received,  $y=0$

- From S3, if 0 input goes to S1; if 1 input goes to S4

- S4: the 4 desired sequence 0101 is received,  $y=0$

- From S4, if 0 input goes to S3; if 1 input goes to S0


 


FIGURE 7.17

State Graph of 0101 Sequence Detector Design with Moore FSM
 
## 7.3.3.2 Moore State and Transition Tables of 0101 Sequence Detector

- State table
- Transition table
  - In this design, a 3-bit register is required to encode the four states.
  - Furthermore, the last column of both tables indicates that the output ``y" is solely determined by the current state, regardless of the input ``x".



cur_state	nxt_state		y
	x=0	x=1	
S0	S1	S0	0
S1	S1	S2	0
S2	S3	S0	0
S3	S1	S4	0
S4	S3	S0	1

(a) State Table of the 0101 Sequence Detector Design with Moore FSM

q2q1q0	q2+q1+q0+		y
	x=0	x=1	
000	001	000	0
001	001	010	0
010	011	000	0
011	001	100	0
100	011	000	1

S0=3'b000, S1=3'b001, S2=3'b010,  
S3=3'b011, S4=3'b100

(b) Transition Table of the 0101 Sequence Detector Design with Moore FSM

**FIGURE 7.18**


State and Transition Tables of 0101 Sequence Detector Design with Moore FSM

## 7.3.3.3 Verilog HDL Design of 0101 Moore Sequence Detector

```

1  module seq_det_0101_moore (input  rst,
2                             input  clk,
3                             input  x ,
4                             output y );
5
6  parameter SIZE = 3;
7  parameter S0 = 3'b000, S1 = 3'b001, S2 = 3'b010,
8             S3 = 3'b011, S4 = 3'b100;
9
10 reg [SIZE-1:0] cur_state; // Sequential part of the FSM
11 reg [SIZE-1:0] nxt_state; // Combinational part of the FSM
12
13 //-----State Register -----
14 always @ (posedge clk, negedge rst) begin
15     if (~rst) begin
16         cur_state <= S0;
17     end else begin
18         cur_state <= nxt_state;
19     end
20 end
21
22 //-----Next state combinational circuit-----
23 always @ (cur_state, x, rst) begin
24     if (~rst) begin
25         nxt_state <= S0;
26     end else begin
27         case(cur_state)
28             S0:    if(~x) nxt_state = S1;
29             S1:    if(x)  nxt_state = S2;
30             S2:    if(x)  nxt_state = S0; else nxt_state = S3;
31             S3:    if(x)  nxt_state = S4; else nxt_state = S1;
32             S4:    if(x)  nxt_state = S0; else nxt_state = S3;
33             default: nxt_state = S0;
34         endcase
35     end
36 end
37
38 //-----Output combinational circuit-----
39 assign y = (cur_state==S4) ;
40 endmodule


```

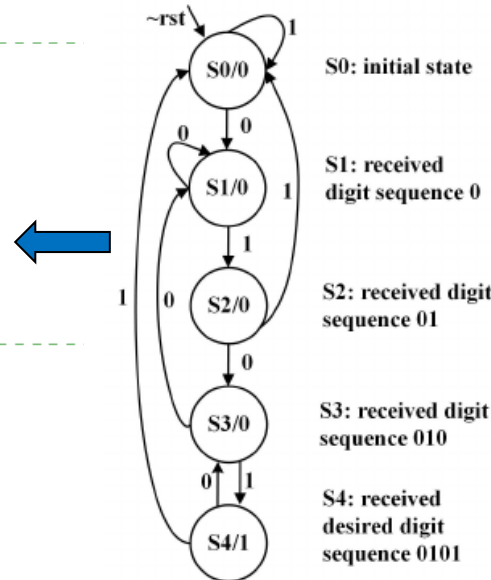


- Verilog code to describe the Moore machine
  - The state register is defined in lines 13-20, while the next state transitions are specified in lines 22-36.
  - In line 39, the output ``y" is activated exclusively when the current state is ``S4". This illustrates the input independence characteristic of a Moore machine.

## 7.3.3.4 Simulation and Synthesis Analysis of 0101 Moore Sequence Detector

### • A. Synthesized Circuit

 

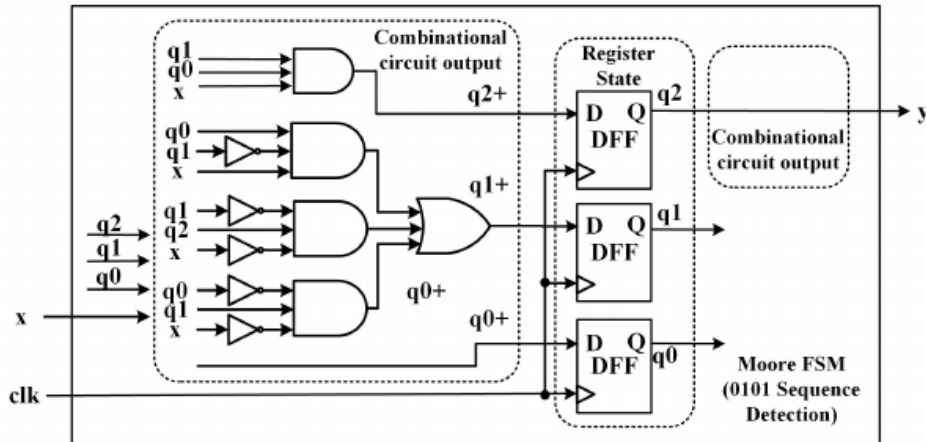(a) K-Map of the 0101 Sequence Detector Design with Moore FSM



(b) Circuit of the 0101 Sequence Detector Design with Moore FSM

cur_state	nxt_state		y
	x=0	x=1	
S0	S1	S0	0
S1	S1	S2	0
S2	S3	S0	0
S3	S1	S4	0
S4	S3	S0	1

(a) State Table of the 0101 Sequence Detector Design with Moore FSM

q2q1q0	q2+q1+q0+		y
	x=0	x=1	
000	001	000	0
001	001	010	0
010	011	000	0
011	001	100	0
100	011	000	1

S0=3'b000, S1=3'b001, S2=3'b010,  
 S3=3'b011, S4=3'b100  
 (b) Transition Table of the 0101 Sequence Detector Design with Moore FSM

FIGURE 7.19


K-Map Optimization and Circuit of 0101 Sequence Detector Design with Moore FSM



## 7.3.3.4 Simulation and Synthesis Analysis of 0101 Moore Sequence Detector
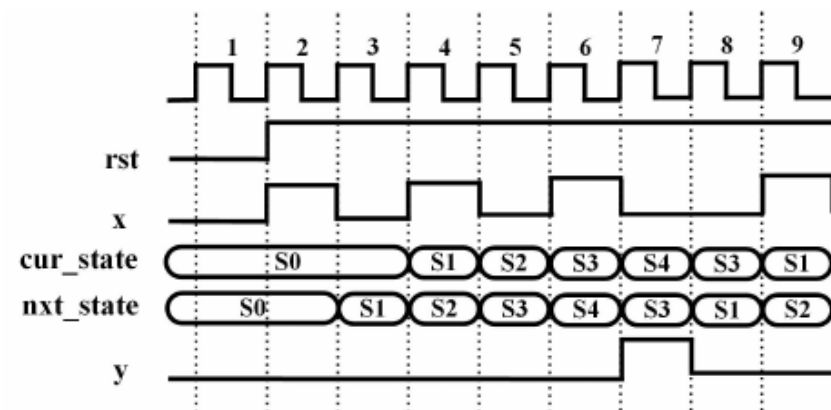
### • B. Timing Diagram

- The sequence detection commences in the second clock cycle, following the reset phase.
- From clock cycles 3 to 5, the input digits ``010" are sequentially received, leading to the machine transitioning to the ``S3" state by clock cycle 6.
- During clock cycle 6, upon receiving the final digit one, the computation of the next state results in ``S4".
- In clock cycle 7, the current state reflects the transition to ``S4", indicating the successful acquisition of the entire digit string ``0101".



cur_state	nxt_state		y
	x=0	x=1	
S0	S1	S0	0
S1	S1	S2	0
S2	S3	S0	0
S3	S1	S4	0
S4	S3	S0	1

(a) State Table of the 0101 Sequence Detector Design with Moore FSM

q2q1q0	q2+q1+q0+		y
	x=0	x=1	
000	001	000	0
001	001	010	0
010	011	000	0
011	001	100	0
100	011	000	1

S0=3'b000, S1=3'b001, S2=3'b010,  
S3=3'b011, S4=3'b100

(b) Transition Table of the 0101 Sequence Detector Design with Moore FSM

FIGURE 7.20

Timing Diagram of 0101 Sequence Detector Design with Moore FSM



7.1 Modeling Finite State Machine

7.2 Mealy and Moore FSMs with Verilog Design


7.3 Design Example: Sequence Detector

**7.4 Design Example: Odd/Even Number of 1's Checker**

7.5 Design Example: Data Package Receiver

## 7.4.1 Introduction to Odd/Even Number of 1's Checker

- Odd/Even Number of 1's Checker
  - A digital circuit that determines whether a given binary sequence contains an odd or even number of 1's.
  - This type of circuit is commonly used in
    - Error detection, parity checking, and data transmission.
  - It is a fundamental components in digital circuit that provides important parity information and is essential for ensuring data integrity in various circuits and systems.

 


**FIGURE 7.21**

Odd/Even Number of 1's Checker

## 7.4.2 State Graph of Odd/Even 1's Checker


- State Graph of Odd/Even 1's Checker
  - It starts in the initial state ``INI``
  - In the ``ODD`` state,
    - The next state remains in ``ODD`` if the input is zero, as the odd count of 1's continues. If the input is one, the graph transitions to the state ``EVEN``, indicating that an even number of 1's is received.
  - In the ``EVEN`` state,
    - The next state stays in ``EVEN`` if the input is zero, while it transitions back to the ``ODD`` state if the input is one.
  - If the enable signal ``en`` is OFF, the state remains unchanged meaning that the circuit is temporarily inactive.
  - If a reset occurs, the state returns to the initial state ``INI``, since the FSM is initiated.

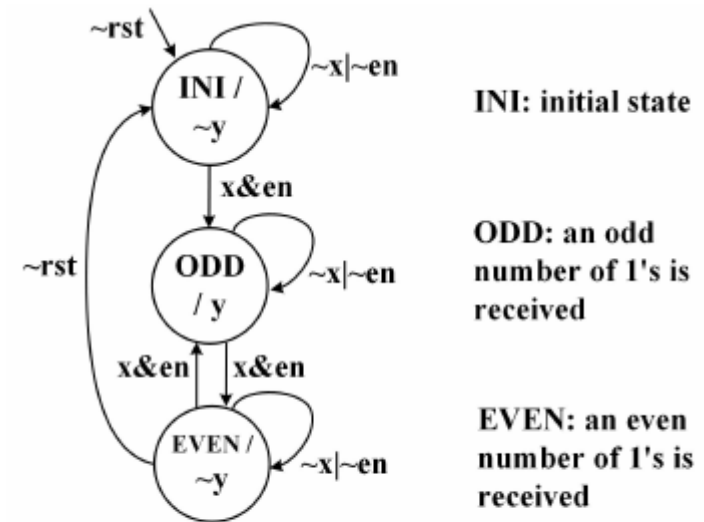

**FIGURE 7.22**  
State Graph of Odd/Even 1's Checker
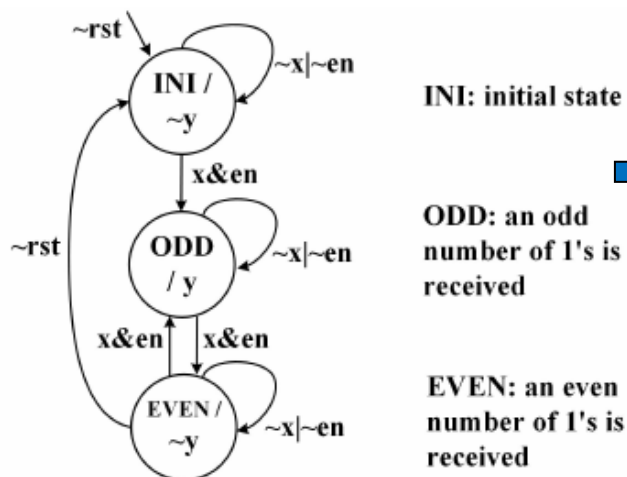
## 7.4.3 State and Transition Tables of Odd/Even 1's Checker

- State and Transition Tables of Odd/Even 1's Checker
  - Next state transitions:
    - If the circuit is disabled, the state remains unchanged in its current state.
    - As the input zero doesn't alter the ODD or EVEN state, the state also remains identical to the current state
    - The state only updates when both the enable ``en" and ``x" inputs are set to ones.
  - The Boolean sum of all the inputs should evaluate to one, as represented by ``en' + x' + en·x = 1".



cur_state	nxt_state (en, x)			y
	~en	~x	en&x	
INI	INI	INI	ODD	0
ODD	ODD	ODD	EVEN	1
EVEN	EVEN	EVEN	ODD	0

(a) State Table of Odd Even 1's Checker

q1q0	q1+q0+ (en, x)			y
	~en	~x	en&x	
00	00	00	01	0
01	01	01	10	1
10	10	10	01	0

INI=2'b00, ODD=2'b01, EVEN=2'b10

(b) Transition Table of Odd Even 1's Checker

**FIGURE 7.23**


State and Transition Tables of Odd/Even 1's Checker

## 7.4.4 Verilog HDL Design of Odd/Even 1's Checker

```

1  module odd_even_1s_checker(input  rst ,
2                             input  clk ,
3                             input  en  ,
4                             input  x   ,
5                             output y   );
6
7  parameter SIZE = 2;
8  parameter INI  = 2'b00, ODD  = 2'b01, EVEN = 2'b10;
9
10 reg [SIZE-1:0] cur_state; // Sequential part of the FSM
11 reg [SIZE-1:0] nxt_state; // Combinational part of the FSM
12
13 //-----State Register -----
14 always @ (posedge clk or negedge rst) begin
15     if (~rst) begin
16         cur_state <= INI ;
17     end else begin
18         cur_state <= nxt_state;
19     end
20 end

```

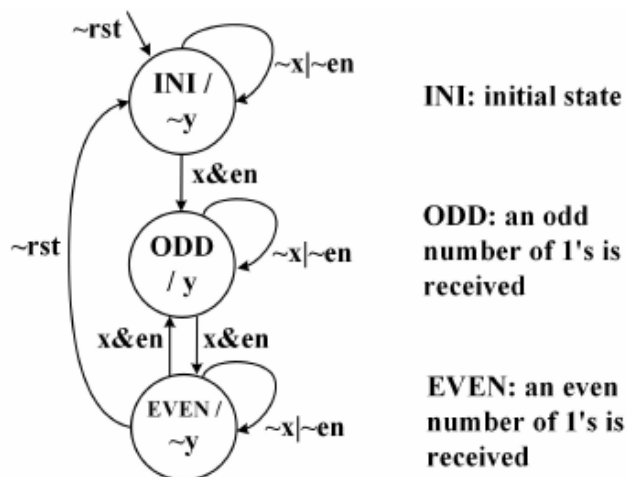


```

21 //-----Next state combinational circuit-----
22 always @ (cur_state, en, x, rst) begin
23     if(~rst) begin
24         nxt_state = INI;
25     end else begin
26         case(cur_state)
27             INI      : if(x&en) nxt_state = ODD ;
28             ODD      : if(x&en) nxt_state = EVEN;
29             EVEN     : if(x&en) nxt_state = ODD ;
30             default  : nxt_state = INI;
31         endcase
32     end
33 end
34
35 //-----Output combinational circuit-----
36 assign y = (cur_state==ODD);
37 endmodule

```

## 7.4.5 Simulation and Synthesis Analysis of Odd/Even 1's Checker

### A. Synthesized Circuit

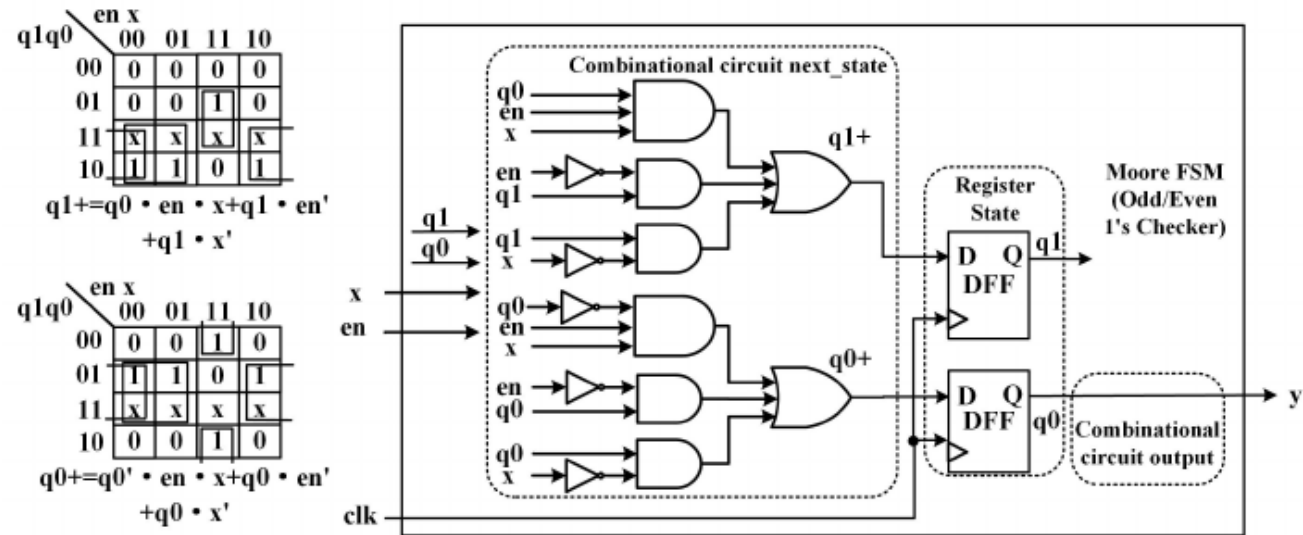

(a) K-Map of Odd Even 1's Checker

(b) Circuit of Odd Even 1's Checker

**FIGURE 7.24**

K-Map Optimization and Circuit of Odd/Even 1's Checker



cur_state	nxt_state (en, x)			y
	~en	~x	en&x	
INI	INI	INI	ODD	0
ODD	ODD	ODD	EVEN	1
EVEN	EVEN	EVEN	ODD	0

q1q0	q1+q0+ (en, x)			y
	~en	~x	en&x	
00	00	00	01	0
01	01	01	10	1
10	10	10	01	0


INI=2'b00, ODD=2'b01, EVEN=2'b10

(a) State Table of Odd Even 1's Checker

(b) Transition Table of Odd Even 1's Checker

## 7.4.5 Simulation and Synthesis Analysis of Odd/Even 1's Checker

### • B. Timing Diagram

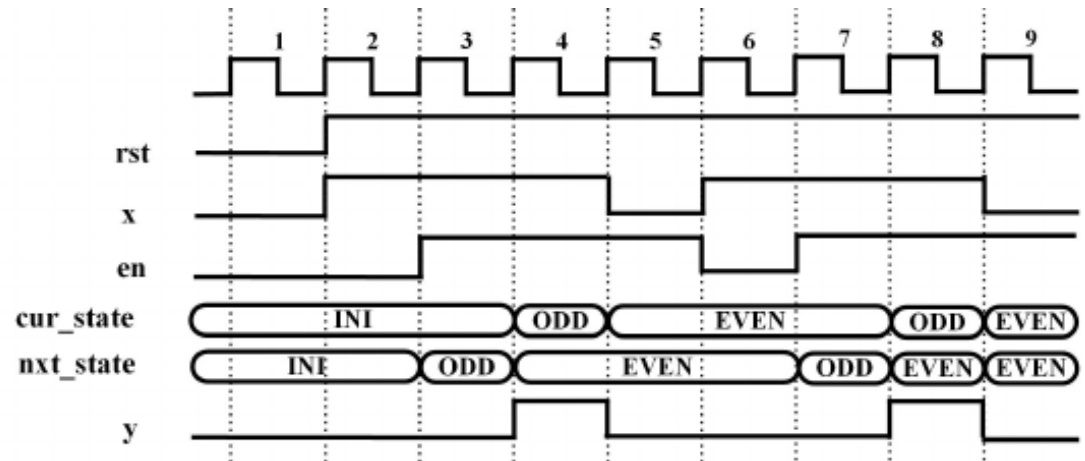

**FIGURE 7.25**

Timing Diagram of Odd/Even 1's Checker



cur_state	nxt_state (en, x)			y
	~en	~x	en&x	
INI	INI	INI	ODD	0
ODD	ODD	ODD	EVEN	1
EVEN	EVEN	EVEN	ODD	0

q1q0	q1+q0+ (en, x)			y
	~en	~x	en&x	
00	00	00	01	0
01	01	01	10	1
10	10	10	01	0

INI=2'b00, ODD=2'b01, EVEN=2'b10

(a) State Table of Odd Even 1's Checker

(b) Transition Table of Odd Even 1's Checker

7.1 Modeling Finite State Machine

7.2 Mealy and Moore FSMs with Verilog Design

7.3 Design Example: Sequence Detector


7.4 Design Example: Odd/Even Number of 1's Checker

**7.5 Design Example: Data Package Receiver**



## 7.5.1 Introduction to Data Package Receiver


- Introduction to Data Package Receiver
  - In the majority of serial bus communications, data is transmitted in the form of packets, which consist of multiple data segments.
  - Data package header, command, and stop tail through the output indicators ``header'', ``cmd'', and ``tail'', respectively.
  - Furthermore, the extracted data from the data package is shown through the output ``rev\_data''.

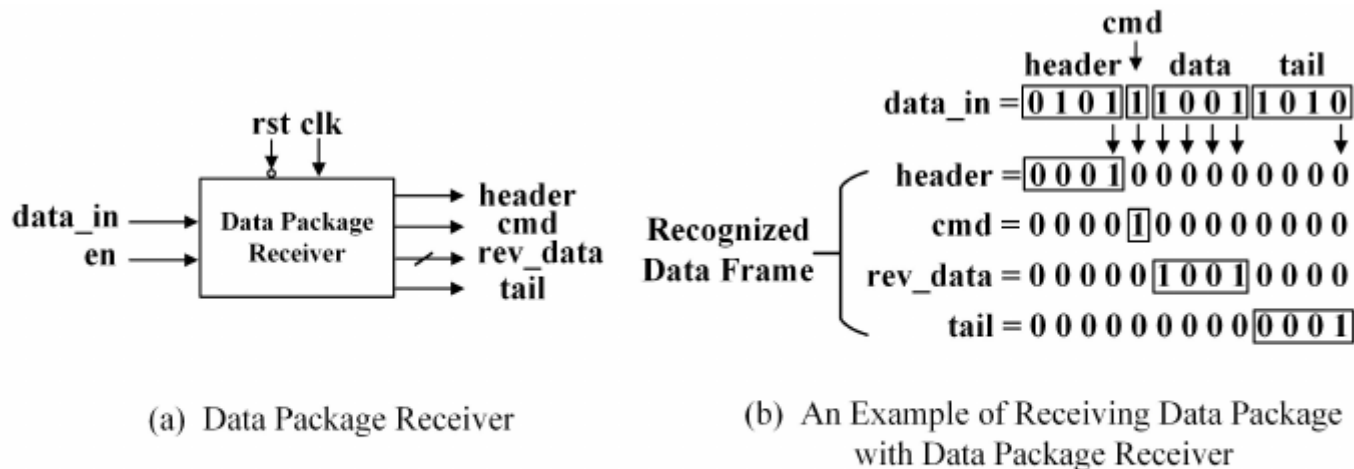

**FIGURE 7.26**  
Data Package Receiver

## 7.5.1 Introduction to Data Package Receiver


- Data Package Receiver
  - Header: a digit string of 0101 represents the start/head of a data package
  - Command: 1 is a write command and 0 is a read command
  - Received data: copy all 4-bit the data as data received
  - Tail: a digit string of 1010 represents an end/tail of a data package, or a data package is successfully received
- Outputs:
  - Header: header received indicator
  - Cmd: command indicator
  - Rev\_data: received 4-bit data
  - Tail: tail received indicator

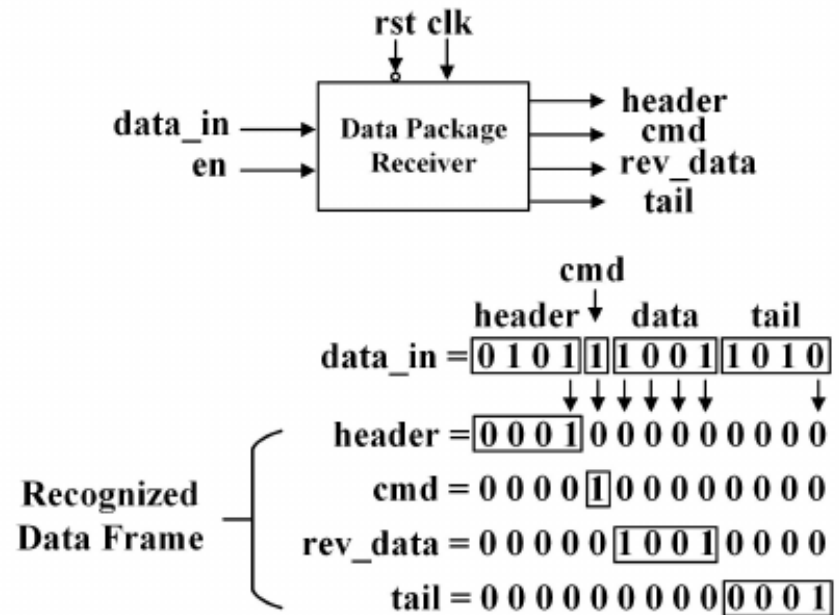

**FIGURE 7.26**  
Data Package Receiver

## 7.5.2 State Graph of Data Package Receiver

- State graph
  - H0: initial state
  - H1-H3: header received
  - CM: command state
  - RD: data receiving state
  - T0: starts detecting tail
  - T1-T3: tail received
- Input and output
  - d: data\_in; serial input
  - h: header; indicator output
  - c: cmd; indicator output
  - r: rev\_data; 4-bit output
  - t: tail; indicator output

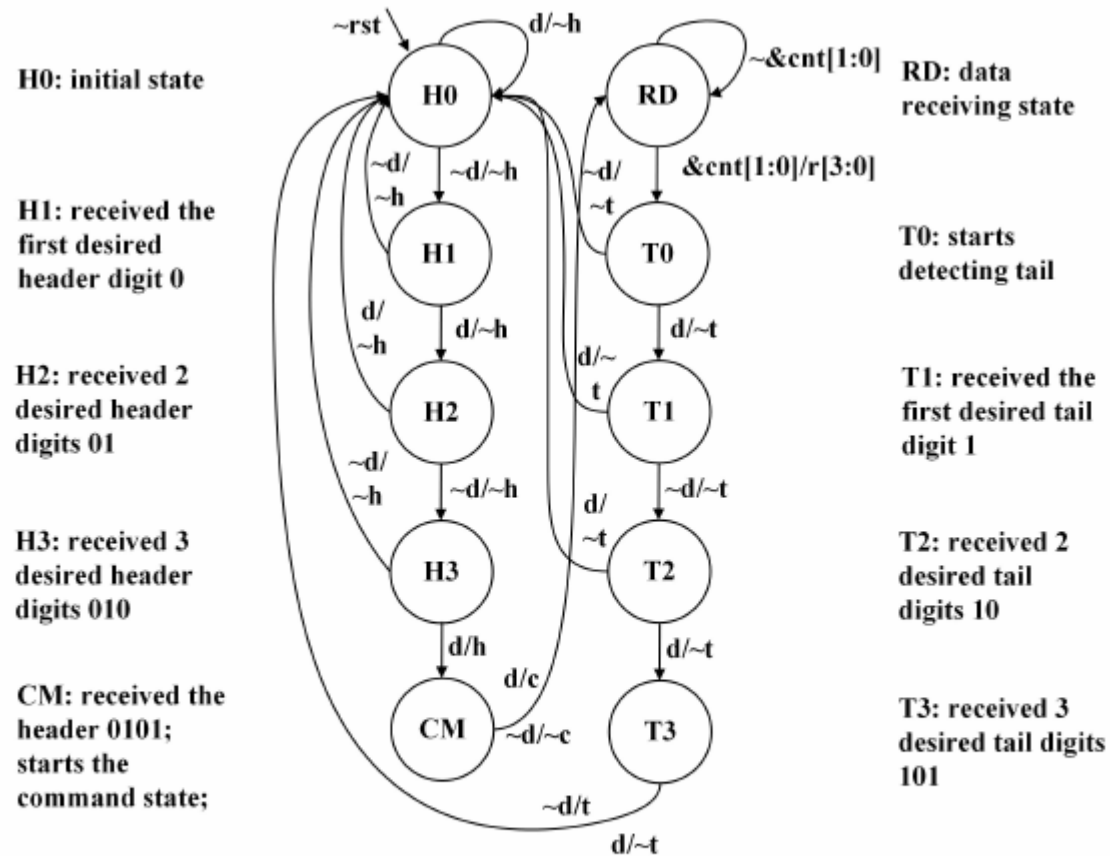

**FIGURE 7.27**  
State Graph of Data Package Receiver

Figure 1. The effect of the number of trials on the number of correct responses. The number of correct responses was significantly higher than the number of incorrect responses in all cases. Error bars represent the standard error of the mean.

- State Table
- Transition Table




**H0: initial state**

H2: received 2  
desired header  
digits 01

**H3: received 3  
desired header  
digits 010**

 **CM: received the header 0101; starts the command state;**



**T1:** received the first desired tail digit 1

**T2: received 2  
desired tail  
digits 10**

**T3: received 3  
desired tail digits  
101**

**FIGURE 7.28**  
State and Transition Tables of Data Package Receiver

FIGURE 7.28

State and Transition Tables of Data Package Receiver

## 7.5.4 Verilog HDL Design of Data Package Receiver

```

1 module data_pack_rec(input          rst          ,
2                       input          clk          ,
3                       input          en           ,
4                       input          data_in      ,
5                       output         header       ,
6                       output         cmd         ,
7                       output reg [3:0] rev_data  ,
8                       output         tail        );

```

```

9 parameter SIZE = 4;
10 parameter H0 = 4'b0000;
11 parameter H1 = 4'b0001;
12 parameter H2 = 4'b0010;
13 parameter H3 = 4'b0011;
14 parameter CM = 4'b0100;
15 parameter RD = 4'b0101;
16 parameter T0 = 4'b0110;
17 parameter T1 = 4'b0111;
18 parameter T2 = 4'b1000;
19 parameter T3 = 4'b1001;

```

```

20
21 reg [SIZE-1:0] cur_state; // Sequential part of the FSM
22 reg [SIZE-1:0] nxt_state; // Combinational part of the FSM

```

```

23
24 //-----State Register -----


```

```

25 always @ (posedge clk, negedge rst) begin
26     if(~rst) begin
27         cur_state <= H0          ;
28     end else begin
29         cur_state <= nxt_state;
30     end
31 end

```

- Sequential part of the FSM

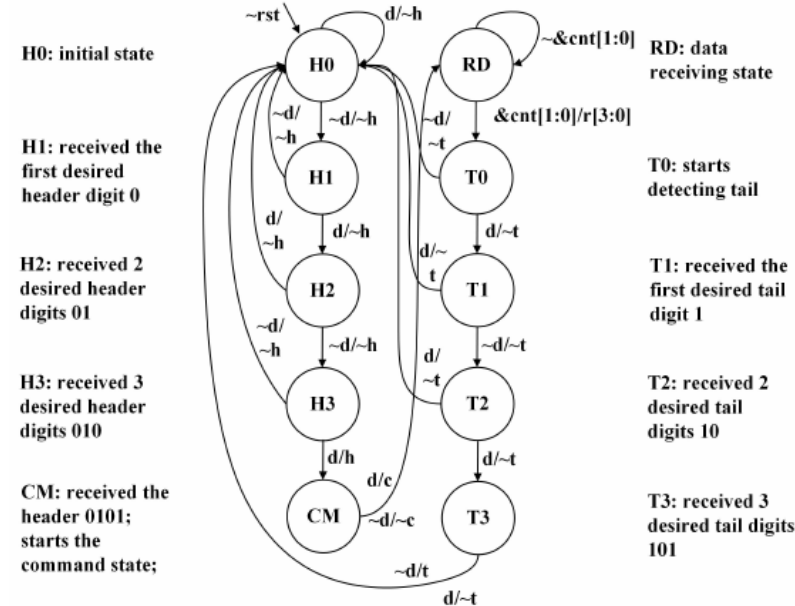


## 7.5.4 Verilog HDL Design of Data Package Receiver

```

33 //-----Next state combinational circuit-----
34 reg [1:0] cnt;
35 wire [1:0] nxt_cnt = (cur_state==RD) ? cnt+2'h1 : 2'h0;
36 always @ (posedge clk, negedge rst) begin
37     if(~rst) begin
38         cnt <= 2'h0 ;
39     end else begin
40         cnt <= nxt_cnt;
41     end
42 end

```

 

**FIGURE 7.29**  
Data Receiver Counter

- Combinational part of the FSM

```


44 always @ (cur_state, en, data_in, rst, cnt) begin
45     if(~rst) begin
46         nxt_state = H0;
47     end else begin
48         case(cur_state)
49             H0      : if(~data_in & en) nxt_state <= H1;
50             H1      : if(data_in )    nxt_state <= H2;
51                     else              nxt_state <= H0;
52             H2      : if(~data_in)     nxt_state <= H3;
53                     else              nxt_state <= H0;
54             H3      : if(data_in )     nxt_state <= CM;
55                     else              nxt_state <= CM;
56             CM      :                  nxt_state <= RD;
57             RD      : if(&cnt)          nxt_state <= T0;
58             T0      : if(data_in)      nxt_state <= T1;
59                     else              nxt_state <= H0;
60             T1      : if(~data_in)     nxt_state <= T2;
61                     else              nxt_state <= H0;
62             T2      : if(data_in)      nxt_state <= T3;
63                     else              nxt_state <= H0;
64             T3      :                  nxt_state <= H0;
65             default : nxt_state = H0;
66         endcase
67     end
68 end

```

## 7.5.4 Verilog HDL Design of Data Package Receiver

- Output part of the FSM

```
70 //-----Output combinational circuit-----
71 assign header = (cur_state==H3) & data_in ;
72 assign cmd     = (cur_state==CM) & data_in ;
73 assign tail    = (cur_state==T3) & ~data_in;
74
75 wire [3:0] nxt_rev_data;
76 assign nxt_rev_data=(cur_state==RD)?{rev_data[2:0],data_in}
77                                     : rev_data;
78 always @ (posedge clk, negedge rst) begin
79     if(~rst) begin
80         rev_data <= 4'h0 ;
81     end else begin
82         rev_data <= nxt_rev_data;
83     end
84 end
85 endmodule
```

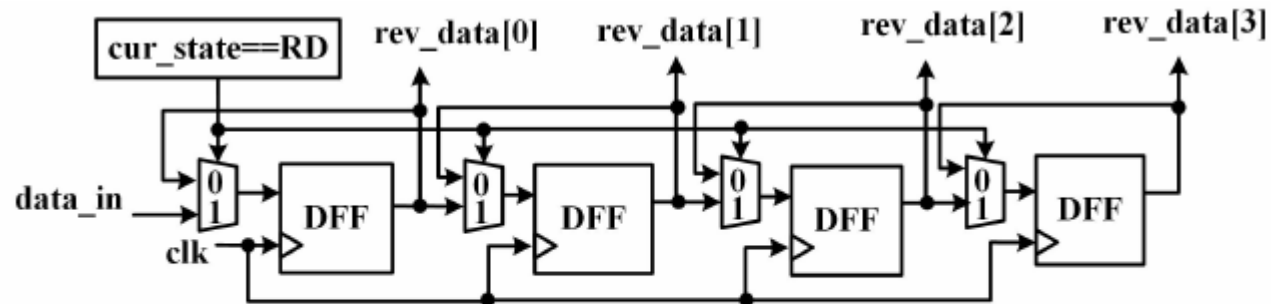


**FIGURE 7.30**  
Data Receiver Shifter



## 7.5.4 Simulation and Synthesis Analysis of Data Package Receiver

- Simulation Analysis

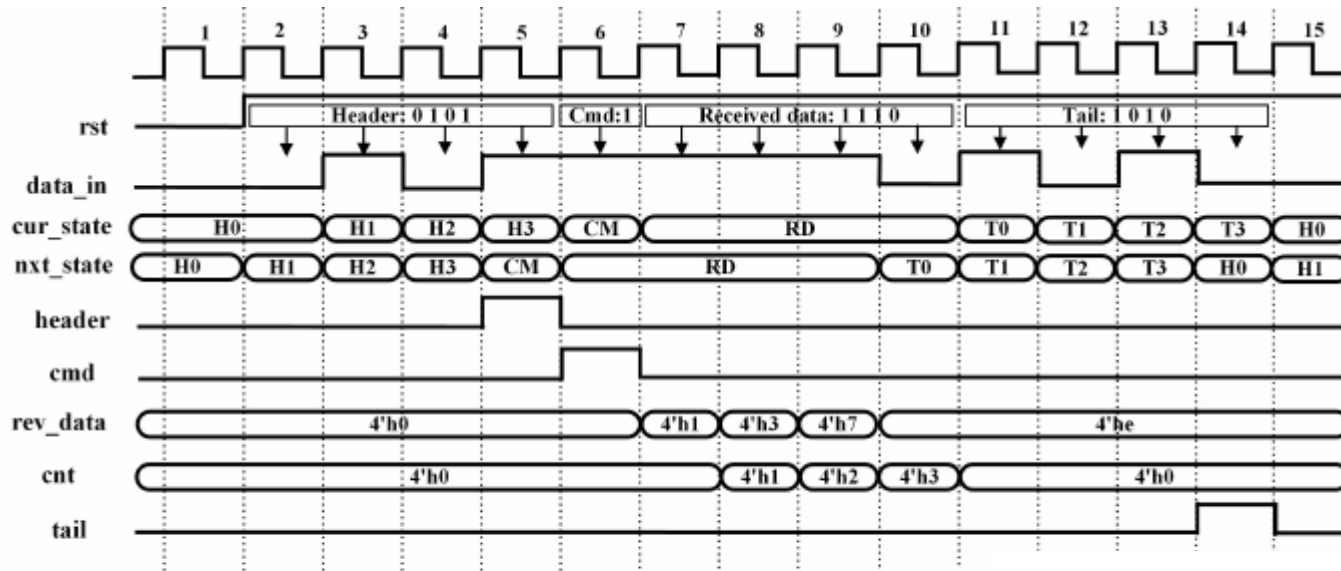

**FIGURE 7.31**  
Timing Diagram of Data Package Receiver

